 


PHYSICAL CELLS - DESIGN FOR MANUFACTURABILITY

- no logic function, (no input) , added to improve yield

TIE CELLS

- Purpose: connect the gate to either V_{DD} / GND (has no input)
- Problem
 - V_{DD} may spike due to ESD
 - these spikes could destroy the thin gate oxide
- solution don't connect gate directly to V_{DD}/GND but have a Tie Cell in between that filters the signal



$$V_g = V_d \rightarrow V_{gs} = V_{ds} \rightarrow V_{ds} > V_{gs} - V_t$$

- NMOS is always in saturation (on) region
- PMOS is always in saturation (on) region
- CMOS gate always connected to V_{DD}
- CMOS gate always connected to V_{SS}/GND




TAP CELLS / WELL TAP

NAND

Purpose: prevent short between V_{DD} to V_{SS} due to latch up issue

   - Problem:
- PNP (PMOS) and NPN (NMOS) junctions are formed which behave like parasitic transistors
 - if both are on, than current flows directly from V_{DD} to GND , likely destroying the transistor
 - this happen if either I_N and $O_U T > V_{DD}$ or I_N and $O_U T < V_{SS}$

- Solution:
- prevent voltage build up by reducing resistance of Nwell (PMOS) and Psubstate
 - increase current path via Tap Cells




END CAP CELLS / BOUNDARY CELLS

- end cap cells ensure continuity of diffusion regions, wells or metal densities

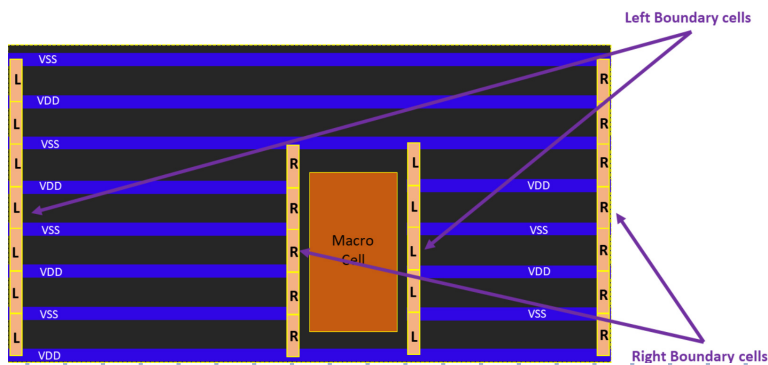- Problems
- standard cells may have open diffusion regions (source/drain regions) that may be floating at the edges → leakage
 - processes like CMP require uniform densities (proportion of diffusion layer coverage per area) (also min/max density constraints must be met)
 - routing of metal at the edge may have unintended parasitic effects
 - uncapped edges introduce parasitics (C, R) that affect signal integrity

Solution: add an end cap cell to both ends of a cell row and around blocks



Random Number Expansion

Data Integrity: Checksum / Error Detection

512 bit not enough : Post Quantum Cryptography

LEF Geometry, Placement rules — NDR

LIB Timing, Voltage, Resistance